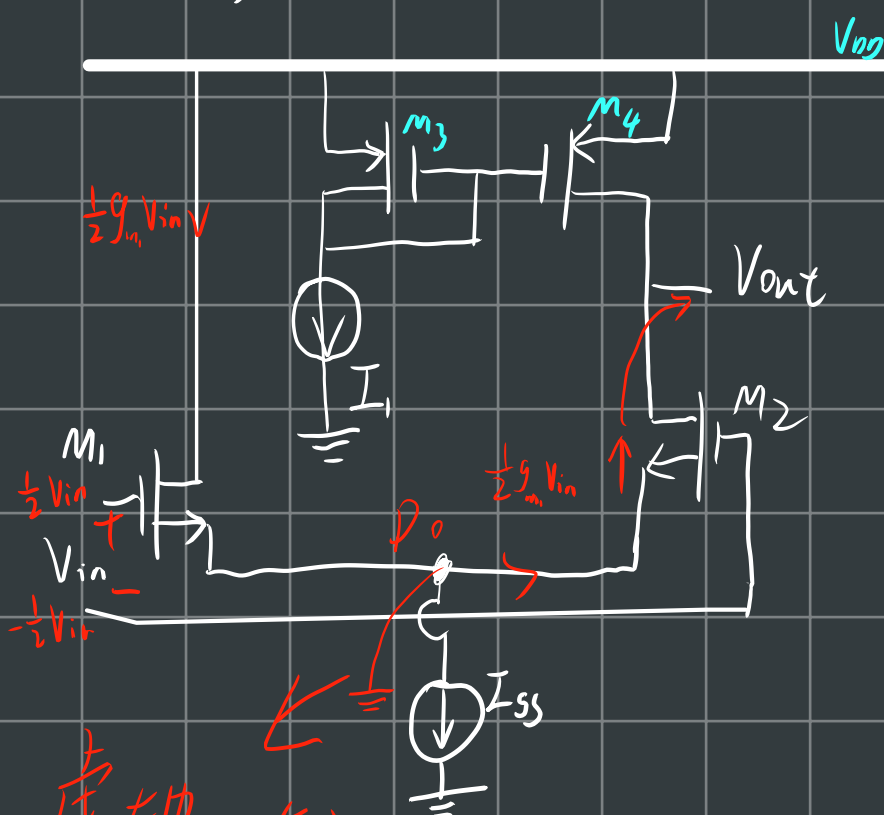


5.7 图中电路 $(\frac{W}{L})_{L4} = \frac{50}{0.5}$ 且 $I_{SS} = 2I_1 = 0.5 \text{ mA}$

(a) 计算小信号电压增益

(b) 如果输入共模电压是 1.3 V , 确定最大输入输出电压摆幅



虚地, 左边电压失效

$$(a) A_v = \frac{V_{out}}{V_{in}} = \frac{V_{out}}{2 \times \frac{V_{in}}{2}}$$

$$= \frac{1}{2} \times (-1) \times \frac{V_{out}}{(-\frac{V_{in}}{2})} = -\frac{1}{2} (-g_{m2} r_{out})$$

$$= +\frac{1}{2} g_{m2} r_{out}$$

$$g_{m1,2} = \sqrt{2K'_1 \left(\frac{W}{L}\right)_1 I_{D1}}$$

$$= 2.345 \text{ mA}$$

$$r_2 = \frac{1}{\frac{0.04}{V} \times 0.25 \text{ mA}} = \dots$$

$$r_4 = \frac{1}{\frac{0.05}{V} \times 0.25 \text{ mA}} = \dots$$

$$R_{out} = (2r_2) // r_4 = \dots$$

求小信号, V_{DD} 点虚地
求内阻, 电流源开路

(b) 在 M_1, M_2 饱和情况下

电压摆幅为 $2 \times (V_{out, \max} - V_{out, \min})$

$$V_{out, \min} = V_{cm} - V_{DS2} + V_{DS2}$$


$$= V_{cm} - V_{th2}$$

$$= 0.6 \text{ V}$$

$$V_{out, \max} = V_{DD} - V_{DS4}$$

$$= V_{DD} - \sqrt{\frac{2I_{D4}}{K'_4 \left(\frac{W}{L}\right)_4 I_{D4}}}$$

$$= \dots$$

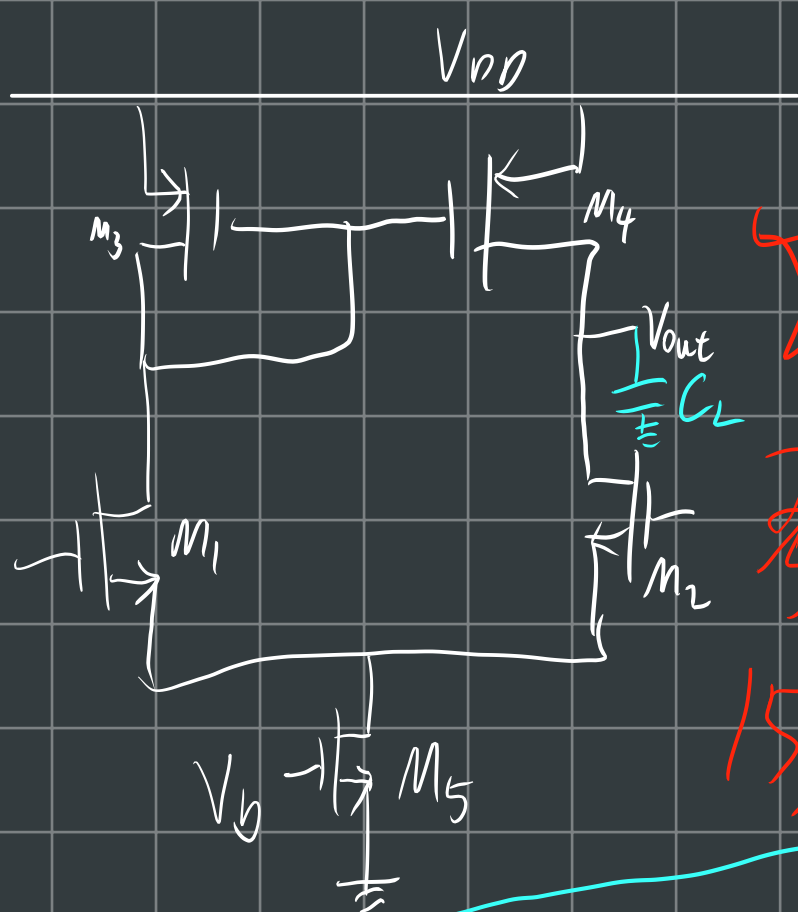

$$V_{DD} = -V_{SS} = 2.5V$$

$$SR \geq 5V/\mu s, C_L = 5pF$$

$$f_{-3dB} \geq 100kHz$$

$$A_V = 100V/V$$

$$-1.5 \leq ICMR \leq 2$$

$$P_{diss} \leq 0.5mW, \lambda_n = 0.04V^{-1}, \lambda_p = 0.05V^{-1}$$



考卷图

15分+

从表达式(简单的)指标或电流入手

$$P_{diss} = I_5 (V_{DD} - V_{SS}) \leq 0.5mW$$

$$I_5 \leq 0.1mA$$

$$\textcircled{1} SR = \frac{I_5}{C_L} = \frac{I_5}{5pF} \geq 5V/\mu s$$

$$I_5 \geq 25\mu A$$

$$\textcircled{2} W_{-3dB} = 2\pi f_{-3dB} = \frac{1}{R_{out} C_L} = \frac{1}{R_{out} \cdot 5pF}$$

$$\Rightarrow f_{-3dB} = \frac{1}{2\pi R_{out} \cdot 5pF} \geq 100kHz$$

$$\Rightarrow R_{out} \leq \frac{1}{2\pi \times 5pF \times 100kHz} = 318k\Omega$$

$$\because R_{out} = \frac{1}{(\lambda_n + \lambda_p) I_5} \leq 318k\Omega$$

$$\Rightarrow I_5 \geq \frac{1}{(\frac{0.04}{V} + \frac{0.05}{V}) \times 318k\Omega} = 35\mu A$$

$$\textcircled{3} P_{diss} = 2V_{DD} I_5 = 5 \times I_5 \leq 0.5mW$$

$$\therefore I_5 \geq 100\mu A$$

综合①②③: $35\mu A \leq I_5 \leq 100\mu A$ 取 $I_5 = 80\mu A$

$$\begin{aligned}
 (4) \quad |A_v| &= g_{m2} (r_{o2} \parallel r_{o4}) \\
 &= \sqrt{2I_2} \frac{1}{K'_2 \left(\frac{W}{L}\right)_2} \times \frac{1}{\left(\frac{0.04}{V} + \frac{0.05}{V}\right) I_2} \\
 &= \sqrt{80\mu A} \frac{110\mu A}{V^2} \left(\frac{W}{L}\right)_2 \times \frac{1}{\frac{0.09}{V} \times 40\mu A} \\
 &= 100 V/V \\
 \Rightarrow \left(\frac{W}{L}\right)_{2,3} &= \frac{14.7 \mu m}{1 \mu m}
 \end{aligned}$$

$$(7) \quad V_b = ?$$

$$\begin{aligned}
 (5) \quad & m_5 \text{ 临界饱和} \\
 V_{in, min} &= V_{S1} + V_{DS1} + V_{GS1} = -1.5 \\
 \Rightarrow -2.5V + \sqrt{\frac{2I_5}{K'_1 \left(\frac{W}{L}\right)_5}} + \left(\sqrt{\frac{2I_1}{K'_1 \left(\frac{W}{L}\right)_1}} + V_{th1}\right) &= -1.5V \\
 \Rightarrow -2.5V + \sqrt{\frac{2 \times 80\mu A}{\frac{110\mu A}{V^2} \times \left(\frac{W}{L}\right)_5}} + \left(\sqrt{\frac{2 \times 40\mu A}{\frac{110\mu A}{V^2} \times 14.7}} + 0.7V\right) &= -1.5 \\
 \Rightarrow \left(\frac{W}{L}\right)_5 &= \frac{239 \mu m}{1 \mu m}
 \end{aligned}$$

$$\begin{aligned}
 (6) \quad & m_{1,2} \text{ 临界饱和} \\
 V_{GS1} &\geq V_{GS1} - V_{th1} \\
 V_{G1} &\leq V_{D1} + V_{th1} \\
 \Rightarrow V_{G1} &\leq (V_{DD} - |V_{GS3}|) + V_{th1} \\
 V_{in, max} &= V_{DD} - |V_{GS3}| + V_{th1} \\
 2V &= 2.5V - \left(\sqrt{\frac{2I_3}{K'_3 \left(\frac{W}{L}\right)_3}} + V_{th3}\right) + V_{th1} \\
 2V &= 2.5V - \left(\sqrt{\frac{2 \times 40\mu A}{\frac{50\mu A}{V^2} \left(\frac{W}{L}\right)_3}} + 0.7V\right) + 0.7V \\
 \Rightarrow \left(\frac{W}{L}\right)_{3,4} &= \frac{6.4 \mu m}{1 \mu m}
 \end{aligned}$$